

Task 1:-

Procedure:

- I drag three resistors and connect them in parallel combination.
- I set the value of R1, R2 & R3 (**10k, 2k and 1k respectively**) according to the circuit.
- Then I connected the **9V** battery in parallel combination with the resistors. I also connect the negative terminal of battery with the ground.
- I connected one ammeter with **R1** , **other** with **R2** and third ammeter with **R3** in series combination to measure current.
- Then I connected voltmeter across **R1**, in parallel combination to measure voltage.
- Then I click the run command button . **Current and voltages** are measured. Practical value was obtained.
- Then I calculate the theoretical value.

Task 2:-

Procedure:

- I drag four resistors and connect them in parallel combination.
- I set the value of R1, R2 , R3 & R4(**100, 3k, 5k and 10k respectively**) according to the circuit.
- Then I connected the **9V** battery in parallel combination with the resistors. I also connect the negative terminal of battery with the ground.

- I connected one ammeter with **R1** , **other** with **R2** ,third ammeter with **R3 and** forth with **R4** in series combination to measure current.
- Then I connected voltmeter across the common points of all resistors , in parallel combination to measure voltage.
- Then I click the run command button . **Current and voltages** are measured. Practical value was obtained.
- Then I calculate the theoretical value.