
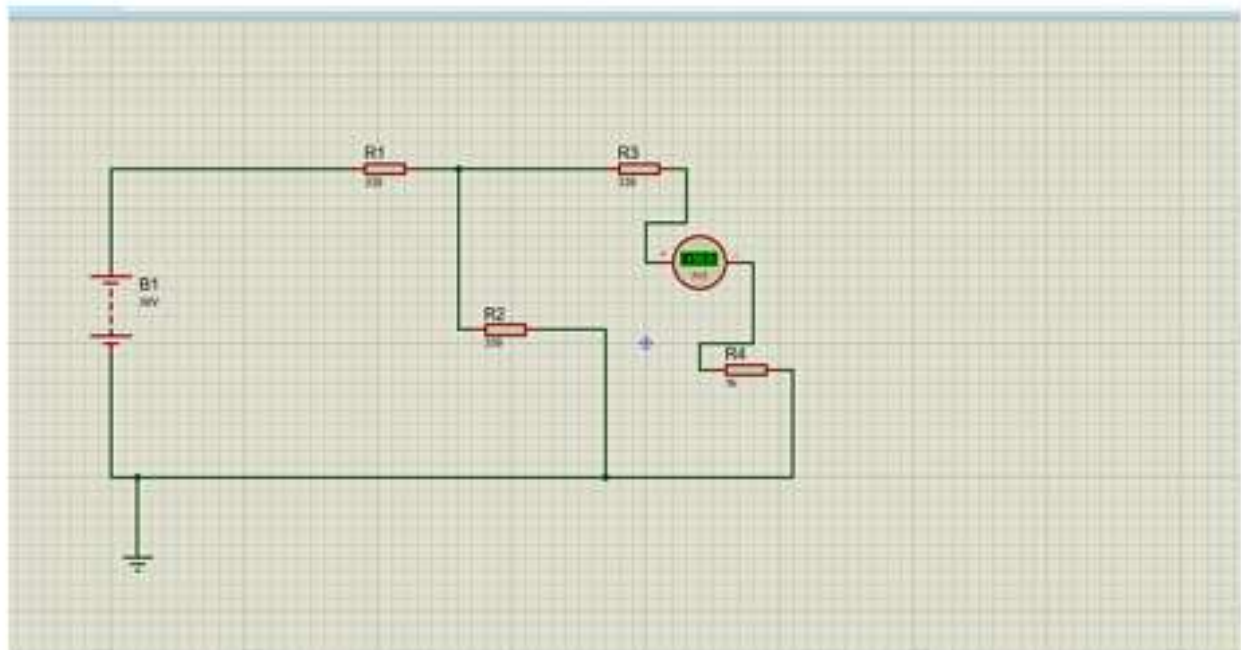


Objective The objective of this lab is verify Thevenin's theorem and to find the full load current..


Circuit - 1: To find load current

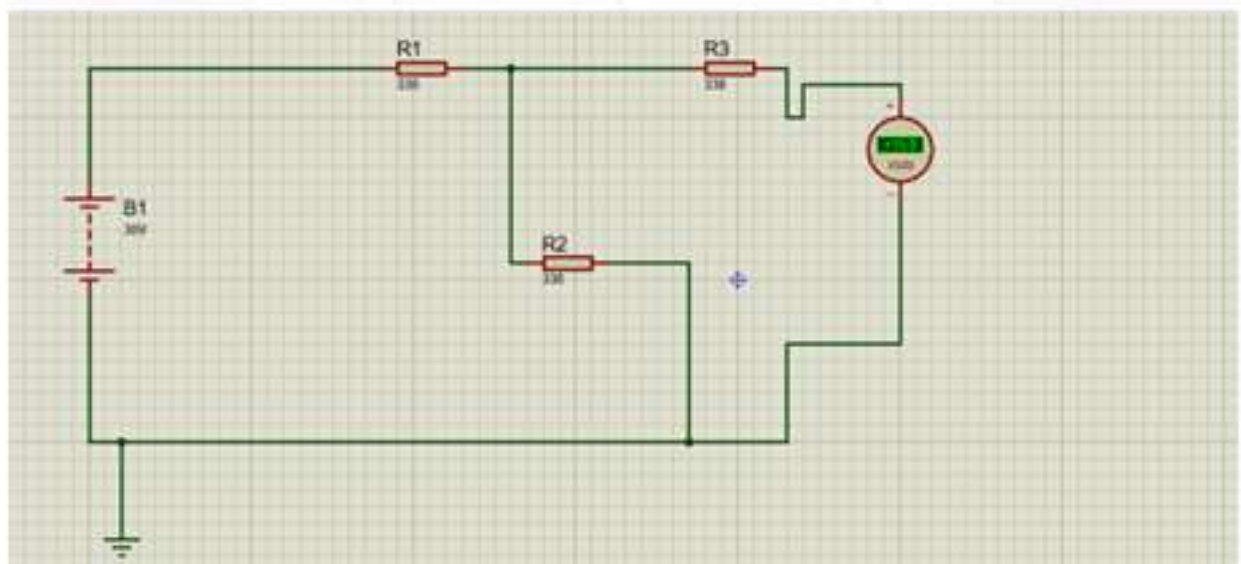

To find VTH:



To find RTH:

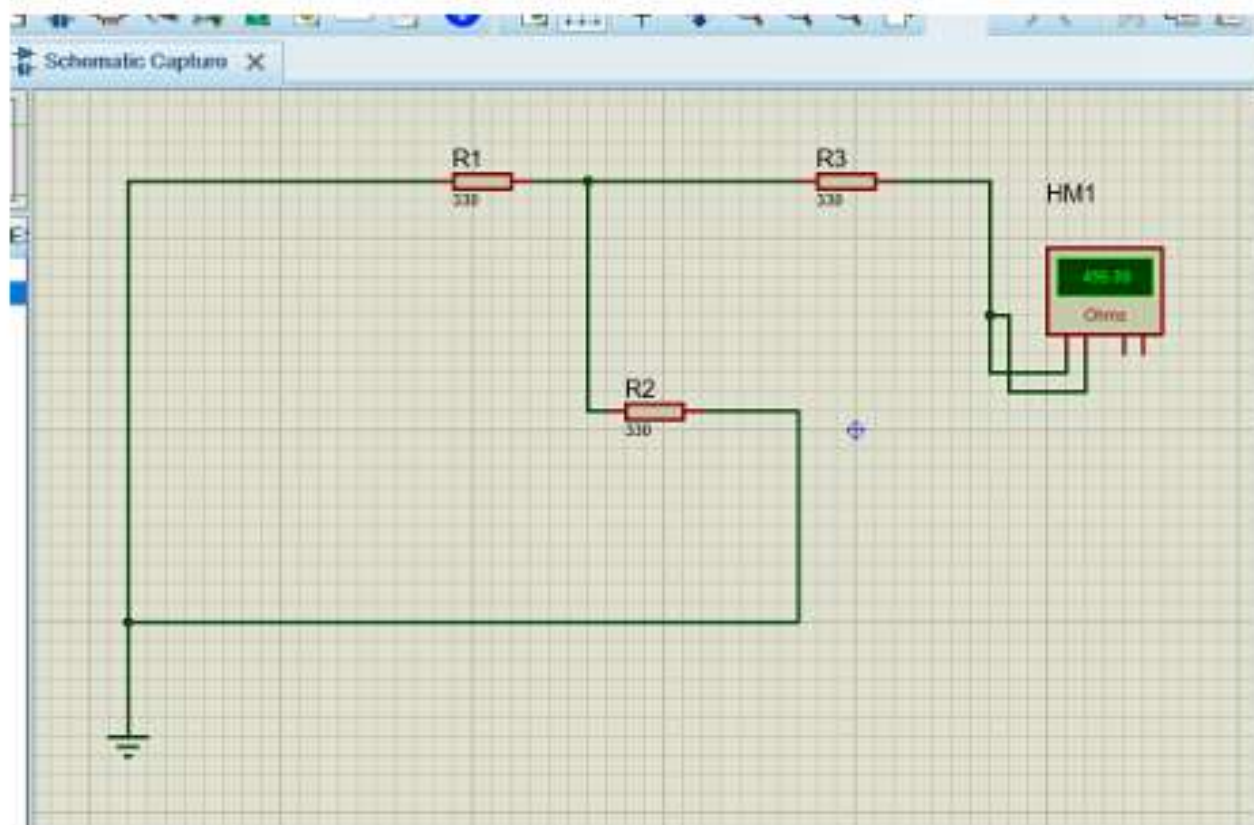

Thevenin's Equivalent circuit:

